

Name _____

Date _____

Period _____


Unit 14
Circuits Practice Test

Form P


1. What is meant when someone says the circuit is “open” or “closed”?
2. Where do the charges come from in an electric circuit?
3. In a circuit, what is the purpose of...
 - a. a battery?
 - b. a resistor?
4. Do batteries supply AC or DC? What is the difference between them?
5. How much power is dissipated by a $500\ \Omega$ resistor with a current of $0.040\ \text{A}$ running through it?
6. Draw a series circuit containing a 6-v battery, a $3\text{-}\Omega$ resistor, a $6\text{-}\Omega$ resistor, and another $6\text{-}\Omega$ resistor.
 - a. How much current is flowing through the $3\text{-}\Omega$ resistor?
 - b. How much power is dissipated by the $3\text{-}\Omega$ resistor?
7. Draw a circuit using the same battery and resistors as above, but with everything in parallel.
 - a. How much current is flowing through the $3\text{-}\Omega$ resistor?
 - b. How much power is dissipated by the $3\text{-}\Omega$ resistor?

8. If the $3\text{-}\Omega$ resistors in Questions 6 and 7 were actually $3\text{-}\Omega$ light bulbs, which one would be brighter? Explain

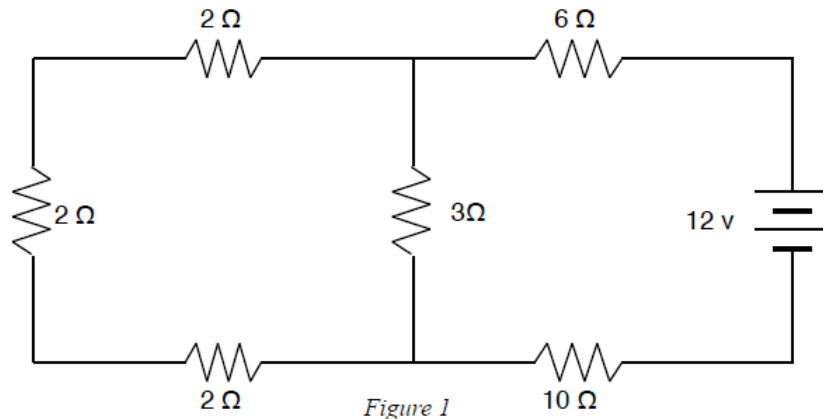9. Use the information given in the circuit diagram in Figure 1 below to find the following:



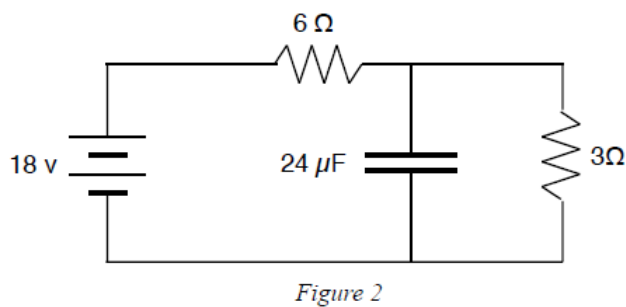- a. How much current flows through the battery?
 - b. What is the voltage drop across the $3\text{-}\Omega$ resistor?
 - c. What is the power dissipated by one of the $2\text{-}\Omega$ resistors?
10. After the battery has been connected for a reasonably long time to the circuit shown in Figure 2 below...



- a. What is the current in the $6\text{-}\Omega$ resistor?
- b. What is the voltage drop across the capacitor?
- c. What is the charge on the capacitor?